



Digital Logic

Lecture Content

- **Boolean Algebra**
- **Gates & Circuits**
- **Combinational Circuits**
- **Minimizing Circuits**
- **Sequential Circuits**



Digital Logic

Learning Objectives

- Understand the basic operations of Boolean algebra
- Distinguish among the different types of flip-flops
- Use Karnaugh maps and the Quine-McCluskey method to simplify Boolean expressions

Boolean Algebra

- Mathematical discipline used to design and analyze the behavior of the digital circuitry in digital computers and other digital systems
 - Named after George Boole
 - Proposed basic principles of the algebra in 1854
- Claude Shannon suggested Boolean algebra could be used to solve problems in relay-switching circuit design
- Is a convenient tool:
 - Analysis: It is an economical way of describing the function of digital circuitry
 - Design: Given a desired function, Boolean algebra can be applied to develop a simplified implementation of that function

Boolean Variables and Operations

- As in any algebra, we have variables and operations
 - A variable may take on the value 1 (TRUE) or 0 (FALSE)
- **AND ($A \cdot B$)**
 - Yields true (binary value 1) if and only if both of its operands are true
 - The AND operation takes precedence over the OR operation
 - Can be represented by simple concatenation instead of the dot operator
- **OR ($A + B$)**
 - Yields true if either or both of its operands are true
- **NOT (\bar{A})**
 - Inverts the value of its operand

Boolean Operators

- With two input variables:

| P | Q | NOT P (\bar{P}) | P AND Q ($P \cdot Q$) | P OR Q ($P + Q$) | P NAND Q ($\overline{P \cdot Q}$) | P NOR Q ($\overline{P + Q}$) | P XOR Q ($P \oplus Q$) |
|---|---|------------------------|----------------------------|-----------------------|--|-----------------------------------|-----------------------------|
| 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 | 0 |

- Extended to more than input variables:

| Operation | Expression | Output = 1 if |
|-----------|------------------------------------|--|
| AND | $A \cdot B \cdot \dots$ | All of the set $\{A, B, \dots\}$ are 1. |
| OR | $A + B + \dots$ | Any of the set $\{A, B, \dots\}$ are 1. |
| NAND | $\overline{A \cdot B \cdot \dots}$ | Any of the set $\{A, B, \dots\}$ are 0. |
| NOR | $\overline{A + B + \dots}$ | All of the set $\{A, B, \dots\}$ are 0. |
| XOR | $A \oplus B \oplus \dots$ | The set $\{A, B, \dots\}$ contains an odd number of 1. |

Basic Algebraic Transformations

| Basic Postulates | | |
|---|--|--------------------|
| $A \cdot B = B \cdot A$ | $A + B = B + A$ | Commutative Laws |
| $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ | $A + (B \cdot C) = (A + B) \cdot (A + C)$ | Distributive Laws |
| $1 \cdot A = A$ | $0 + A = A$ | Identity Elements |
| $A \cdot \bar{A} = 0$ | $A + \bar{A} = 1$ | Inverse Elements |
| Other Identities | | |
| $0 \cdot A = 0$ | $1 + A = 1$ | |
| $A \cdot A = A$ | $A + A = A$ | |
| $A \cdot (B \cdot C) = (A \cdot B) \cdot C$ | $A + (B + C) = (A + B) + C$ | Associative Laws |
| $\overline{A \cdot B} = \bar{A} + \bar{B}$ | $\overline{A + B} = \bar{A} \cdot \bar{B}$ | DeMorgan's Theorem |









Digital Logic

Lecture Content






- Boolean Algebra
- **Gates & Circuits**
- Combinational Circuits
- Minimizing Circuits
- Sequential Circuits

Basic Electronic Circuits

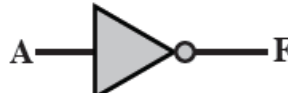- A gate is an electronic circuit that produces an output signal that is a simple Boolean operation on its input signals.
- We say that to **assert** a signal is to cause a signal line to make a transition from its logically false (0) state to its logically true (1) state.

| Name | Graphical Symbol | Algebraic Function | Truth Table | | | | | | | | | | | | | | | |
|------|---|--------------------------------------|--|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| AND |  | $F = A \cdot B$ or $F = AB$ | <table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> | A | B | F | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| A | B | F | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | |
| OR |  | $F = A + B$ | <table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> | A | B | F | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| A | B | F | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | |
| NOT |  | $F = \overline{A}$ or $F = A'$ | <table><tr><th>A</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table> | A | F | 0 | 1 | 1 | 0 | | | | | | | | | |
| A | F | | | | | | | | | | | | | | | | | |
| 0 | 1 | | | | | | | | | | | | | | | | | |
| 1 | 0 | | | | | | | | | | | | | | | | | |
| NAND |  | $F = \overline{AB}$ | <table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> | A | B | F | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| A | B | F | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | |
| NOR |  | $F = \overline{A + B}$ | <table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> | A | B | F | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| A | B | F | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | |
| XOR |  | $F = A \oplus B$ | <table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> | A | B | F | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| A | B | F | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | |

Using NAND and NOR Only

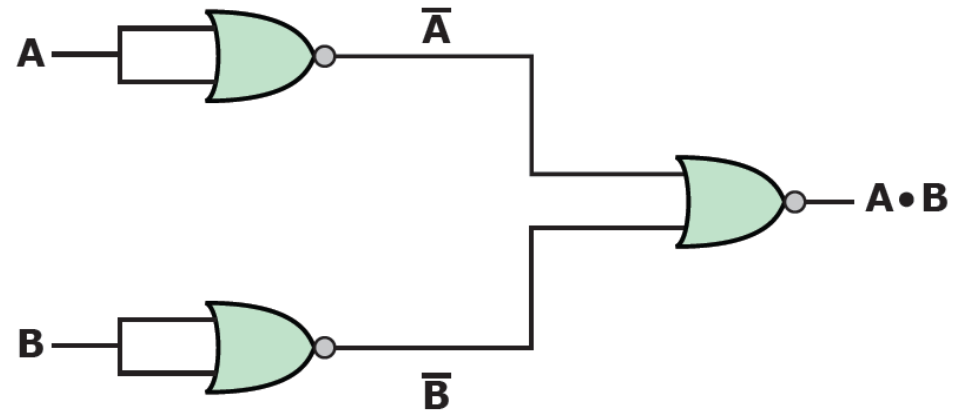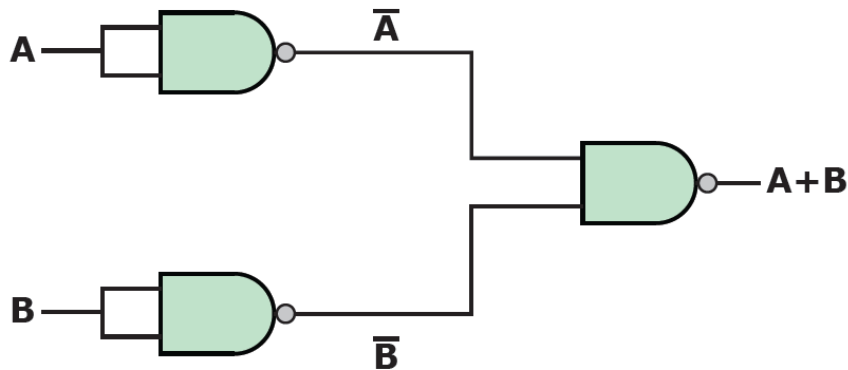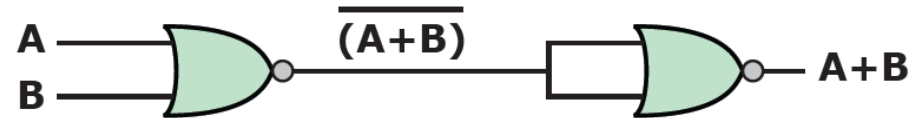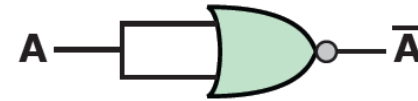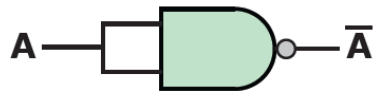



Digital Logic

Lecture Content

- Boolean Algebra
- Gates & Circuits
- **Combinational Circuits**
- Minimizing Circuits
- Sequential Circuits

Combinational Circuits

- An interconnected set of gates whose output at any time is a function only of the input at that time
 - The appearance of the input is followed almost immediately by the appearance of the output, with only gate delays
 - Consists of n binary inputs and m binary outputs
- Can be defined in three ways:
 - Truth table
 - For each of the 2^n possible combinations of input signals, the binary value of each of the m output signals is listed
 - Graphical symbols
 - The interconnected layout of gates is depicted
 - Boolean equations
 - Each output signal is expressed as a Boolean function of its input signals

Small Example: A Truth Table

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Small Example: Boolean Function

- We can transform the truth table easily into a boolean expression
 - We simply look at the position where F is true:
 - $\bar{A}B\bar{C}$
 - $\bar{A}BC$
 - $AB\bar{C}$

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Small Example: Boolean Function

- We can transform the truth table easily into a boolean expression
 - We simply look at the position where F is true:
 - $\bar{A}B\bar{C}$
 - $\bar{A}BC$
 - $AB\bar{C}$
 - This results in the following expression:


$$F = \bar{A}B\bar{C} + \bar{A}BC + AB\bar{C}$$

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

- This is called **Sum of Products (SOP)**

Small Example: Circuit Implementation

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

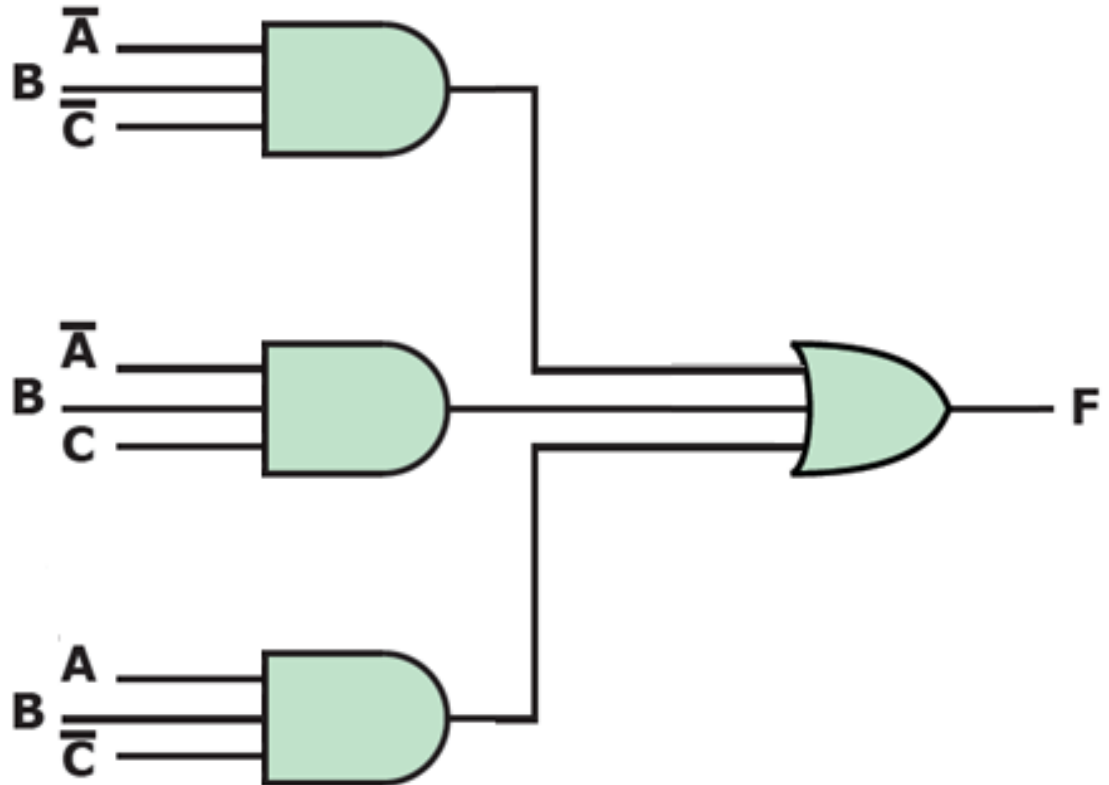

Small Example: Another Boolean Expression

- We could also look at the positions where F is false:
 - $\bar{A}\bar{B}\bar{C}$
 - $\bar{A}\bar{B}C$
 - $A\bar{B}\bar{C}$
 - $A\bar{B}C$
 - $\bar{A}B\bar{C}$

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Small Example: Another Boolean Expression

- We could also look at the positions where F is false:
 - $\bar{A}\bar{B}\bar{C}$
 - $\bar{A}\bar{B}C$
 - $A\bar{B}\bar{C}$
 - $A\bar{B}C$
 - $\bar{A}B\bar{C}$
- The output is 1 when all of these terms are false:

$$F = \overline{(\bar{A}\bar{B}\bar{C})} \cdot \overline{(\bar{A}\bar{B}C)} \cdot \overline{(A\bar{B}\bar{C})} \cdot \overline{(A\bar{B}C)} \cdot \overline{(\bar{A}B\bar{C})}$$

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Small Example: Another Boolean Expression

- We can also say that the output is 1 if none of the input combination producing 0 is true:
 - $\bar{A}\bar{B}\bar{C}$
 - $\bar{A}\bar{B}C$
 - $A\bar{B}\bar{C}$
 - $A\bar{B}C$
 - ABC
- The output is 1 when all of these terms are false:
$$F = \overline{(\bar{A}\bar{B}\bar{C})} \cdot \overline{(\bar{A}\bar{B}C)} \cdot \overline{(A\bar{B}\bar{C})} \cdot \overline{(A\bar{B}C)} \cdot \overline{(ABC)}$$
- Following DeMorgan:

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

$$F = (A + B + C) \cdot (A + B + \bar{C}) \cdot (\bar{A} + B + C) \cdot (\bar{A} + B + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{C})$$




Digital Logic

Lecture Content

- Boolean Algebra
- Gates & Circuits
- Combinational Circuits
- **Minimizing Circuits**
- Sequential Circuits

Small Example: Circuit Implementation

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

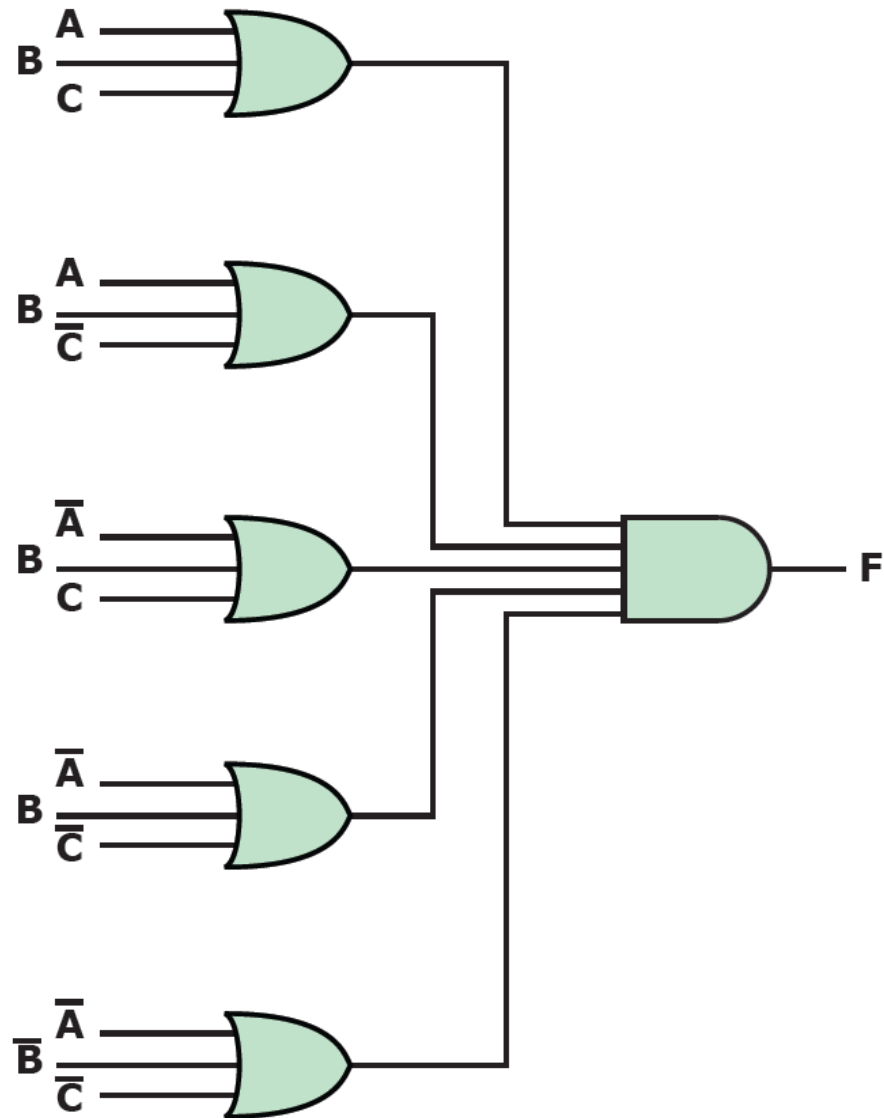

Small Example: Another Boolean Expression



- The last function is called **Product of Sums (POS)**
- Observations:
 - There are several possibilities to express the same function
 - Some are more clever than others
- Considerations:
 - We could use the function with less gates
 - Or it may be preferable to use only NANDs or NORs
- But very often, there is an much smaller expression than SOP or POS

Small Example: Simplified Implementation

- The given Function can also be expressed as

$$F = B(\bar{A} + \bar{C})$$


| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

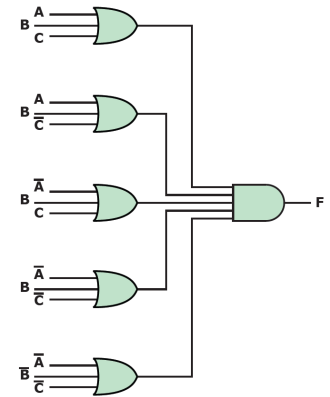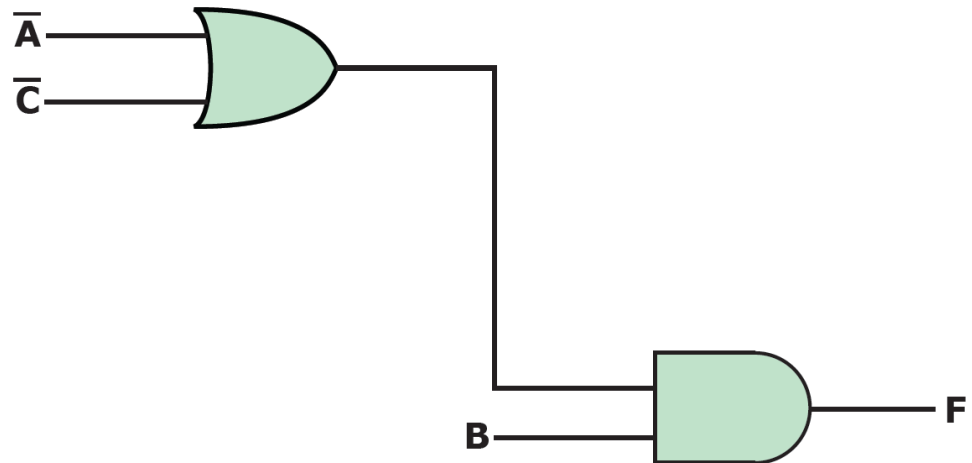




How to Find Simplified Expressions

- By algebraic simplifications
 - Kind of cumbersome, hard to find
- **Karnaugh Maps**
 - Very easy
 - Only up to 4 variables (more are possible but then it gets complicated again)
- **Quine-McCluskey Tables**
 - Algorithmic Approach
 - Works for more than four variables

Karnaugh Maps

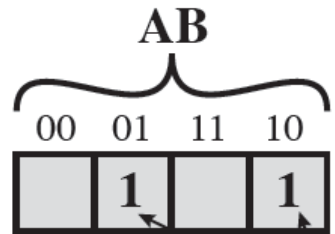

(a) $F = A\bar{B} + \bar{A}B$

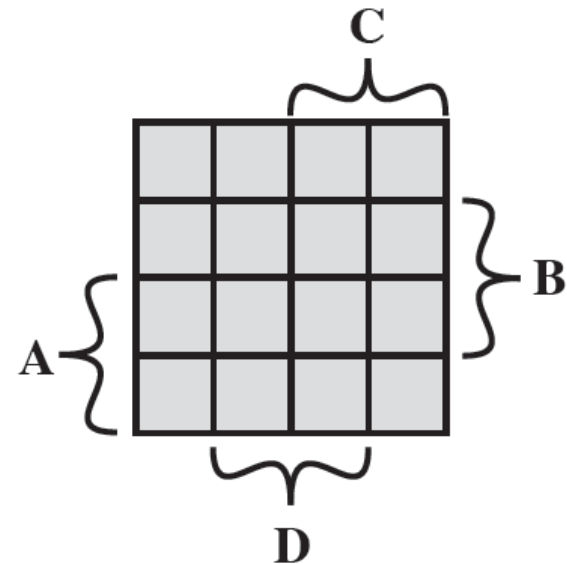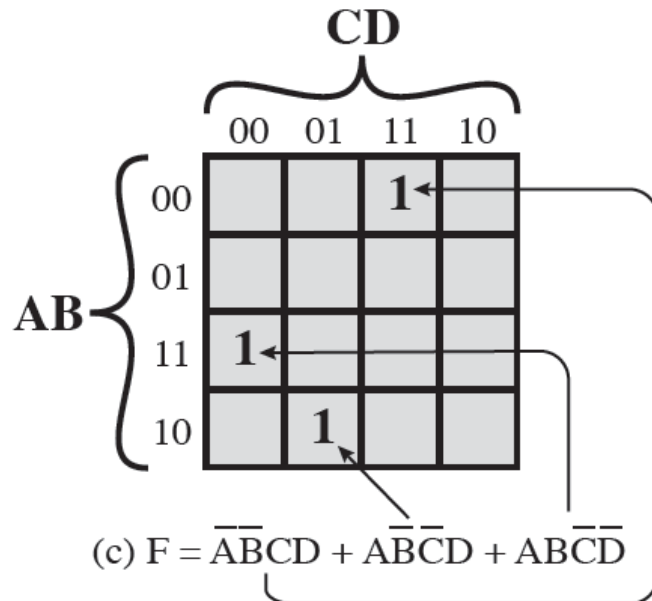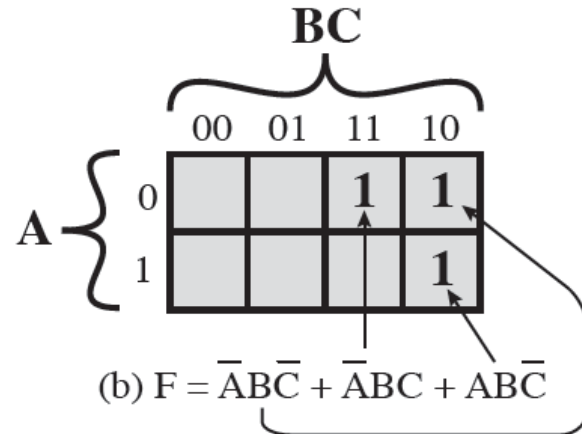


(d) Simplified Labeling of Map


Karnaugh Maps: How Does This Help Us?

- The Maps show the variables and their connection
- We can write a simple algebraic expression by looking at the arrangement of the 1s on the map
- Observation:
 - Whenever two 1s are adjacent, then the corresponding product terms differ in only one variable.
 - In such a case, the two terms can be merged by eliminating that variable.
- Example:


$$RX + R\bar{X} = R$$

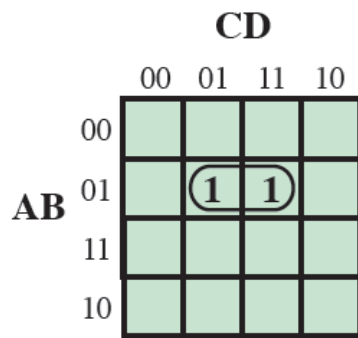


(a) $\bar{A}BD$

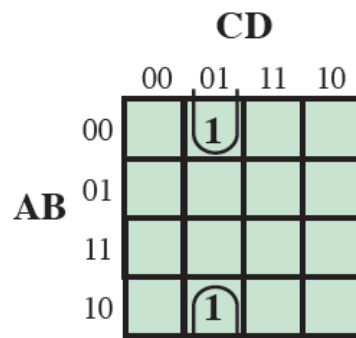


(b) $\bar{B}\bar{C}D$

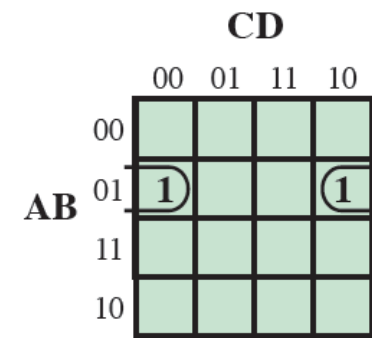


(c) $\bar{A}B\bar{D}$

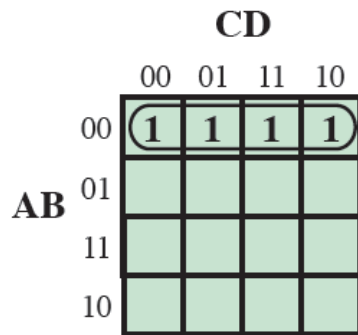


(d) $\bar{A}\bar{B}$

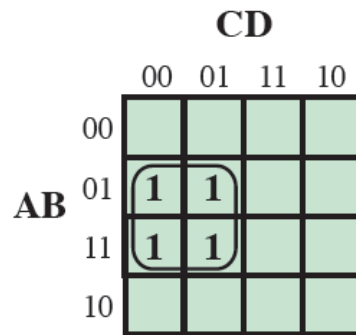


(e) $B\bar{C}$

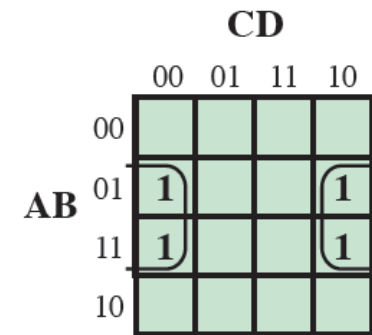


(f) $B\bar{D}$

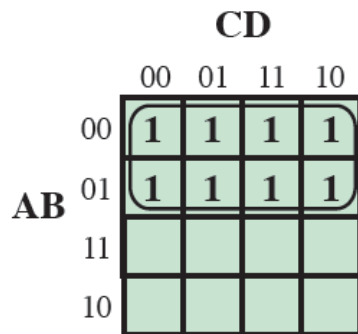

(g) \bar{A}

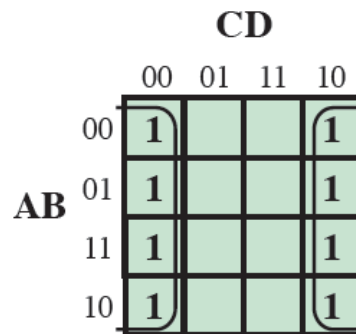

(h) \bar{D}

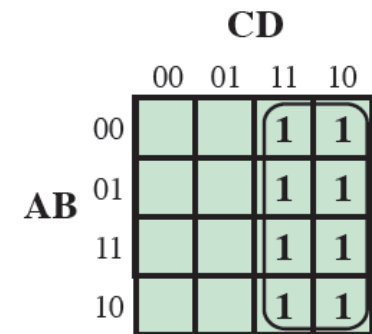


(i) C

Karnaugh Maps: Usage

- Find the largest block of size 1, 2, 4, or 8 in each dimension
- Select additional blocks (as large as possible and as few as possible) until all 1s are marked
- No non-1 must be selected
- Each one can be member of several blocks
- Write down the equation corresponding to the blocks

Karnaugh Maps: Our Example

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

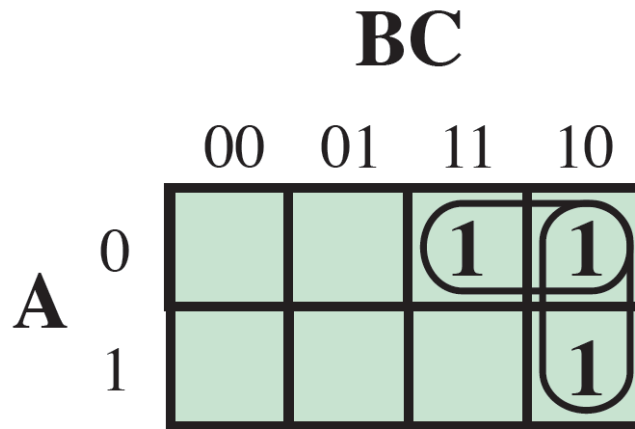


(a) $F = \bar{A}B + B\bar{C}$

Another Example: Decimal Incrementer


| Input | | | | | Output | | | | |
|--------|---|---|---|---|--------|---|---|---|---|
| Number | A | B | C | D | Number | W | X | Y | Z |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 2 | 0 | 0 | 1 | 0 |
| 2 | 0 | 0 | 1 | 0 | 3 | 0 | 0 | 1 | 1 |
| 3 | 0 | 0 | 1 | 1 | 4 | 0 | 1 | 0 | 0 |
| 4 | 0 | 1 | 0 | 0 | 5 | 0 | 1 | 0 | 1 |
| 5 | 0 | 1 | 0 | 1 | 6 | 0 | 1 | 1 | 0 |
| 6 | 0 | 1 | 1 | 0 | 7 | 0 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 8 | 1 | 0 | 0 | 0 |
| 8 | 1 | 0 | 0 | 0 | 9 | 1 | 0 | 0 | 1 |
| 9 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| | 1 | 0 | 1 | 0 | | d | d | d | d |
| | 1 | 0 | 1 | 1 | | d | d | d | d |
| | 1 | 1 | 0 | 0 | | d | d | d | d |
| | 1 | 1 | 0 | 1 | | d | d | d | d |
| | 1 | 1 | 1 | 0 | | d | d | d | d |
| | 1 | 1 | 1 | 1 | | d | d | d | d |

Don't care!


Karnaugh Maps: Decimal Incrementer

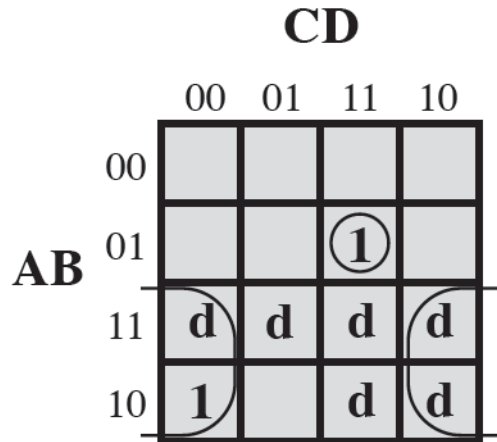


(a) $W = A\bar{D} + \bar{A}BCD$

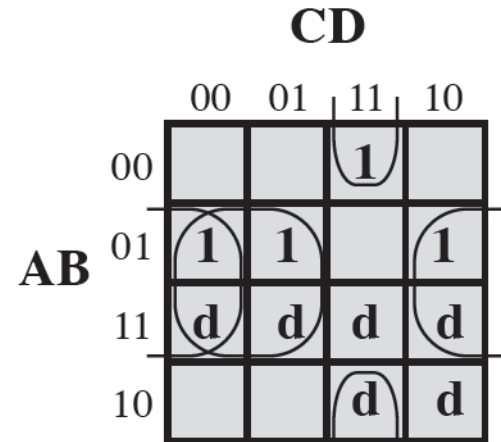

(b) $X = B\bar{D} + B\bar{C} + BCD$

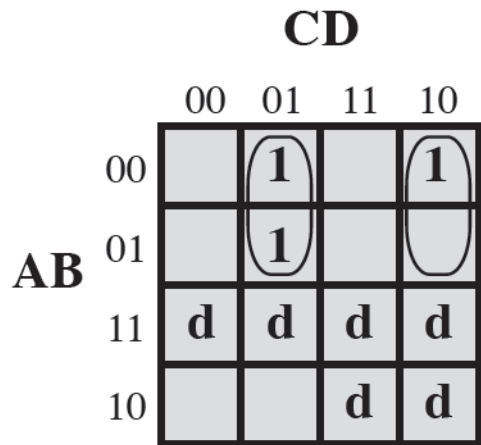

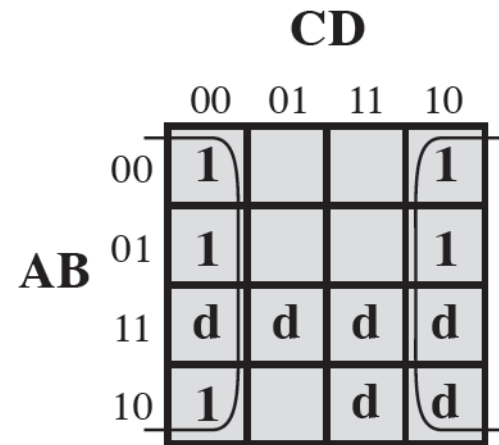(c) $Y = \bar{A}\bar{C}D + \bar{A}C\bar{D}$



(d) $Z = \bar{D}$

The Quine-McCluskey Method

- The Karnaugh Maps are very inconvenient for more than 4 variables
- Other methods are required: The Quine-McCluskey Method
- Let's assume we have the following term:

$$\begin{aligned} F &= ABCD + AB\bar{C}D + AB\bar{C}\bar{D} + A\bar{B}CD + \bar{A}BCD \\ &+ \bar{A}BC\bar{D} + \bar{A}B\bar{C}D + \bar{A}\bar{B}\bar{C}D \end{aligned}$$

The Quine-McCluskey Method

- In the first step, we order the terms in groups:
 - We count the number of complemented variables
 - Terms with the same number of complemented variables form a group

$\overline{A}\overline{B}\overline{C}D$

$AB\overline{C}\overline{D}$

$AB\overline{C}D$

$ABCD$

$\overline{A}BC\overline{D}$

$A\overline{B}CD$

$\overline{A}B\overline{C}D$

$\overline{A}BCD$

- We now look for term differing in only one variable
- They can be replaced by one term without the differing variable
- Because of the ordering: Potential terms can only be in the group to the right

The Quine-McCluskey Method

$\bar{A}\bar{B}\bar{C}D$

$AB\bar{C}\bar{D}$

$AB\bar{C}D$

$ABCD$

$\bar{A}BC\bar{D}$

$A\bar{B}CD$

$\bar{A}B\bar{C}D$

$\bar{A}BCD$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$

$AB\overline{C}\overline{D}$

$AB\overline{C}D$

$ABCD$

$\overline{A}BC\overline{D}$

$A\overline{B}CD$

$\overline{A}B\overline{C}D$

$\overline{A}BCD$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$

$AB\overline{C}\overline{D}$

$AB\overline{C}D$

$ABCD$

$\overline{A}BC\overline{D}$

$A\overline{B}CD$

$\overline{A}B\overline{C}D$

$\overline{A}BCD$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$

$AB\overline{C}\overline{D}$

$AB\overline{C}D$

$ABCD$

$\overline{A}BC\overline{D}$

$A\overline{B}CD$

$\overline{A}B\overline{C}D$

$\overline{A}BCD$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$

$AB\overline{C}D$

$ABCD$

$\overline{A}BC\overline{D}$

$A\overline{B}CD$

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$

$\overline{A}\overline{C}D$

The Quine-McCluskey Method

$\bar{A}\bar{B}\bar{C}D$ ✓

$AB\bar{C}\bar{D}$

$AB\bar{C}D$

$ABCD$

$\bar{A}BC\bar{D}$

$A\bar{B}CD$

$\bar{A}B\bar{C}D$ ✓

$\bar{A}BCD$

$\bar{A}\bar{C}D$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$AB\overline{C}D$ ✓

$ABCD$

$\overline{A}BC\overline{D}$

$A\overline{B}CD$

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$

$\overline{A}\overline{C}D$

$AB\overline{C}$

The Quine-McCluskey Method

$\bar{A}\bar{B}\bar{C}D$ ✓

$AB\bar{C}\bar{D}$ ✓

$AB\bar{C}D$ ✓

$ABCD$

$\bar{A}BC\bar{D}$

$A\bar{B}CD$

$\bar{A}B\bar{C}D$ ✓

$\bar{A}BCD$

$\bar{A}\bar{C}D$

$AB\bar{C}$

The Quine-McCluskey Method

$\bar{A}\bar{B}\bar{C}D$ ✓

$AB\bar{C}\bar{D}$ ✓

$AB\bar{C}D$ ✓

$ABCD$

$\bar{A}BC\bar{D}$

$A\bar{B}CD$

$\bar{A}B\bar{C}D$ ✓

$\bar{A}BCD$

$\bar{A}\bar{C}D$

$AB\bar{C}$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$AB\overline{C}D$ ✓

$ABCD$

$\overline{A}BC\overline{D}$

$A\overline{B}CD$

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$

$\overline{A}\overline{C}D$

$AB\overline{C}$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$AB\overline{C}D$ ✓

$ABCD$

$\overline{A}BC\overline{D}$

$A\overline{B}CD$

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$

$\overline{A}\overline{C}D$

$AB\overline{C}$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$AB\overline{C}D$ ✓

$ABCD$

$\overline{A}BC\overline{D}$

$A\overline{B}CD$

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$

$\overline{A}\overline{C}D$

$AB\overline{C}$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$AB\overline{C}D$ ✓

$ABCD$

$\overline{A}BC\overline{D}$ ✓

$A\overline{B}CD$

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$ ✓

$\overline{A}\overline{C}D$

$AB\overline{C}$

$\overline{A}BC$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$\textcolor{red}{AB}\overline{C}D$ ✓

$ABCD$

$\overline{A}BC\overline{D}$ ✓

$A\overline{B}CD$

$\textcolor{red}{\overline{A}B}\overline{C}D$ ✓

$\overline{A}BCD$ ✓

$\overline{A}\overline{C}D$

$AB\overline{C}$

$\overline{A}BC$

$\textcolor{red}{B}\overline{C}D$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$AB\overline{C}D$ ✓

$ABCD$

$\overline{A}BC\overline{D}$ ✓

$A\overline{B}CD$

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$ ✓

$\overline{A}\overline{C}D$

$AB\overline{C}$

$\overline{A}BC$

$B\overline{C}D$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$AB\overline{C}D$ ✓

$ABCD$

$\overline{A}BC\overline{D}$ ✓

$A\overline{B}CD$

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$ ✓

$\overline{A}\overline{C}D$

$AB\overline{C}$

$\overline{A}BC$

$B\overline{C}D$

$\overline{A}BD$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$AB\overline{C}D$ ✓

$ABCD$ ✓

$\overline{A}BC\overline{D}$ ✓

$A\overline{B}CD$

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$ ✓

$\overline{A}\overline{C}D$

$AB\overline{C}$

ABD

$\overline{A}BC$

$B\overline{C}D$

$\overline{A}BD$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$AB\overline{C}D$ ✓

$ABCD$ ✓

$\overline{A}BC\overline{D}$ ✓

$A\overline{B}CD$ ✓

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$ ✓

$\overline{A}\overline{C}D$

$AB\overline{C}$

ABD

$\overline{A}BC$

ACD

$B\overline{C}D$

$\overline{A}BD$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$AB\overline{C}D$ ✓

$ABCD$ ✓

$\overline{A}BC\overline{D}$ ✓

$A\overline{B}CD$ ✓

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$ ✓

$\overline{A}\overline{C}D$

$AB\overline{C}$

ABD

$\overline{A}BC$

ACD

$B\overline{C}D$

BCD

$\overline{A}BD$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D \checkmark$

$AB\overline{C}\overline{D} \checkmark$

$AB\overline{C}D \checkmark$

$ABCD \checkmark$

$\overline{A}BC\overline{D} \checkmark$

$A\overline{B}CD \checkmark$

$\overline{A}B\overline{C}D \checkmark$

$\overline{A}BCD \checkmark$

$\overline{A}\overline{C}D$

$AB\overline{C}$

ABD

$\overline{A}BC$

ACD

$B\overline{C}D$

BCD

$\overline{A}BD$

The Quine-McCluskey Method

$\overline{A}\overline{B}\overline{C}D$ ✓

$AB\overline{C}\overline{D}$ ✓

$AB\overline{C}D$ ✓

$ABCD$ ✓

$\overline{A}BC\overline{D}$ ✓

$A\overline{B}CD$ ✓

$\overline{A}B\overline{C}D$ ✓

$\overline{A}BCD$ ✓

$\overline{A}\overline{C}D$

$AB\overline{C}$

ABD ✓

$\overline{A}BC$

ACD

$B\overline{C}D$ ✓

BCD ✓

$\overline{A}BD$ ✓

BD

The Quine-McCluskey Method

$\bar{A}\bar{B}\bar{C}D$ ✓

$AB\bar{C}\bar{D}$ ✓

$AB\bar{C}D$ ✓

$ABCD$ ✓

$\bar{A}BC\bar{D}$ ✓

$A\bar{B}CD$ ✓

$\bar{A}B\bar{C}D$ ✓

$\bar{A}BCD$ ✓

$\bar{A}\bar{C}D$

$AB\bar{C}$

ABD ✓

$\bar{A}BC$

ACD

$B\bar{C}D$ ✓

BCD ✓

$\bar{A}BD$ ✓

BD

The Quine-McCluskey Method

- We have already reduced the number of terms to 5:

$$F = BD + \bar{A}\bar{C}D + \bar{A}BC + AB\bar{C} + ACD$$

- Some of might still be redundant

| | $ABCD$ | $AB\bar{C}D$ | $AB\bar{C}\bar{D}$ | $A\bar{B}CD$ | $\bar{A}BCD$ | $\bar{A}BC\bar{D}$ | $\bar{A}\bar{B}CD$ | $\bar{A}\bar{B}\bar{C}D$ |
|-------------------|--------|--------------|--------------------|--------------|--------------|--------------------|--------------------|--------------------------|
| BD | | | | | | | | |
| $\bar{A}\bar{C}D$ | | | | | | | | |
| $\bar{A}BC$ | | | | | | | | |
| $AB\bar{C}$ | | | | | | | | |
| ACD | | | | | | | | |

The Quine-McCluskey Method

- First, we mark all those cells which intersecting terms are compatible
- That is, the variables in the row have the same value as in the column

| | $ABCD$ | $AB\bar{C}D$ | $AB\bar{C}\bar{D}$ | $A\bar{B}CD$ | $\bar{A}BCD$ | $\bar{A}BC\bar{D}$ | $\bar{A}\bar{B}CD$ | $\bar{A}\bar{B}\bar{C}D$ |
|-------------------|--------|--------------|--------------------|--------------|--------------|--------------------|--------------------|--------------------------|
| BD | 0 | 0 | | | 0 | | 0 | |
| $\bar{A}\bar{C}D$ | | | | | | | 0 | 0 |
| $\bar{A}BC$ | | | | | 0 | 0 | | |
| $AB\bar{C}$ | | 0 | 0 | | | | | |
| ACD | 0 | | | 0 | | | | |

The Quine-McCluskey Method

- Now, we mark all those o's, which are alone in their column:

| | $ABCD$ | $AB\bar{C}D$ | $AB\bar{C}\bar{D}$ | $A\bar{B}CD$ | $\bar{A}BCD$ | $\bar{A}BC\bar{D}$ | $\bar{A}\bar{B}CD$ | $\bar{A}\bar{B}\bar{C}D$ |
|-------------------|--------|--------------|--------------------|--------------|--------------|--------------------|--------------------|--------------------------|
| BD | 0 | 0 | | | 0 | | 0 | |
| $\bar{A}\bar{C}D$ | | | | | | | 0 | X |
| $\bar{A}BC$ | | | | | 0 | X | | |
| $AB\bar{C}$ | | 0 | X | | | | | |
| ACD | 0 | | | X | | | | |

The Quine-McCluskey Method

- Now, we mark all those x in which row there is already a marked x:

| | $ABCD$ | $AB\bar{C}D$ | $AB\bar{C}\bar{D}$ | $A\bar{B}CD$ | $\bar{A}BCD$ | $\bar{A}BC\bar{D}$ | $\bar{A}\bar{B}CD$ | $\bar{A}\bar{B}\bar{C}D$ |
|-------------------|----------|--------------|--------------------|--------------|--------------|--------------------|--------------------|--------------------------|
| BD | 0 | 0 | | | 0 | | 0 | |
| $\bar{A}\bar{C}D$ | | | | | | | X | X |
| $\bar{A}BC$ | | | | | X | X | | |
| $AB\bar{C}$ | | X | X | | | | | |
| ACD | X | | | X | | | | |

The Quine-McCluskey Method

- If all columns are covered, we have a final result:

$$F = \bar{A}\bar{C}D + \bar{A}BC + AB\bar{C} + ACD$$



- If there would be an uncovered column, we have to select further rows until all rows are covered

| | $ABCD$ | $AB\bar{C}D$ | $AB\bar{C}\bar{D}$ | $A\bar{B}CD$ | $\bar{A}BCD$ | $\bar{A}BC\bar{D}$ | $\bar{A}\bar{B}CD$ | $\bar{A}\bar{B}\bar{C}D$ |
|-------------------|--------|--------------|--------------------|--------------|--------------|--------------------|--------------------|--------------------------|
| BD | 0 | 0 | | | 0 | | 0 | |
| $\bar{A}\bar{C}D$ | | | | | | | X | X |
| $\bar{A}BC$ | | | | | X | X | | |
| $AB\bar{C}$ | | X | X | | | | | |
| ACD | X | | | X | | | | |


Some More Important Circuits

- Multiplexer:
 - Connects multiple inputs to one output.
 - At any time, only one input is connected to the output
 - Used for signal or data routing
- Decoder:
 - Has a number of output lines of which only one is asserted
 - Generally, they have n inputs and 2^n output lines
- Adders:
 - Pretty obvious


A Multiplexer

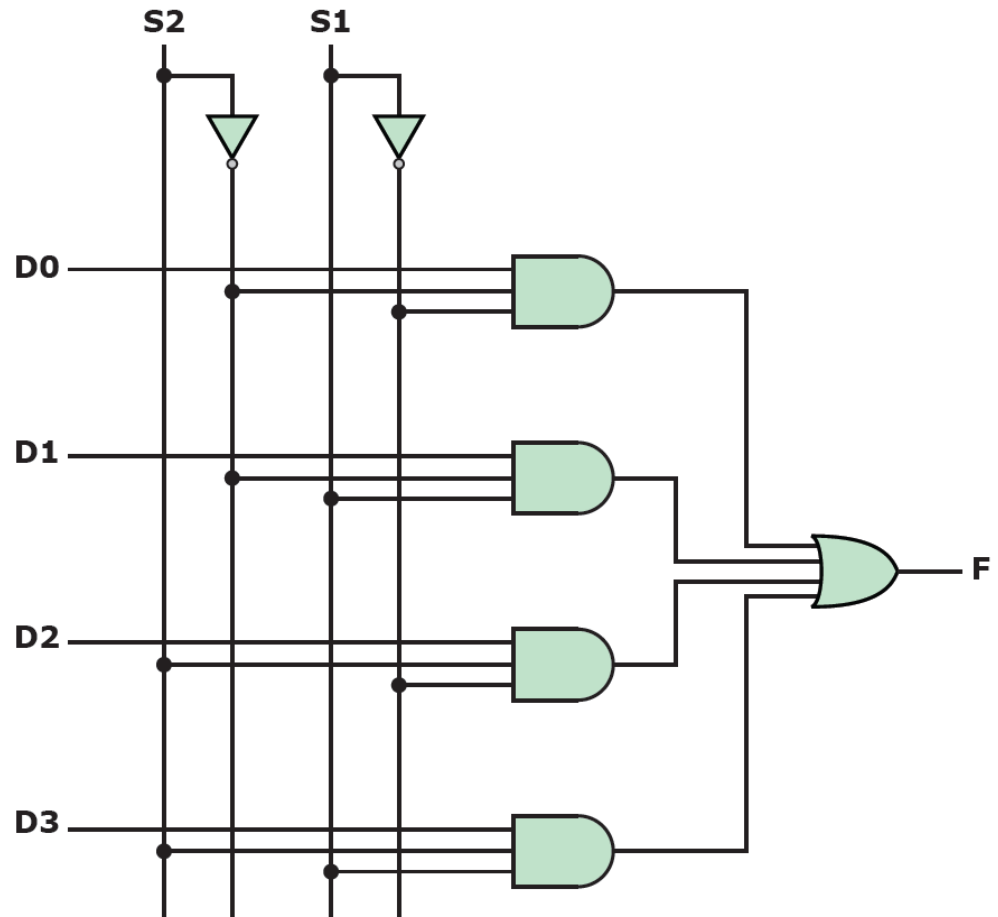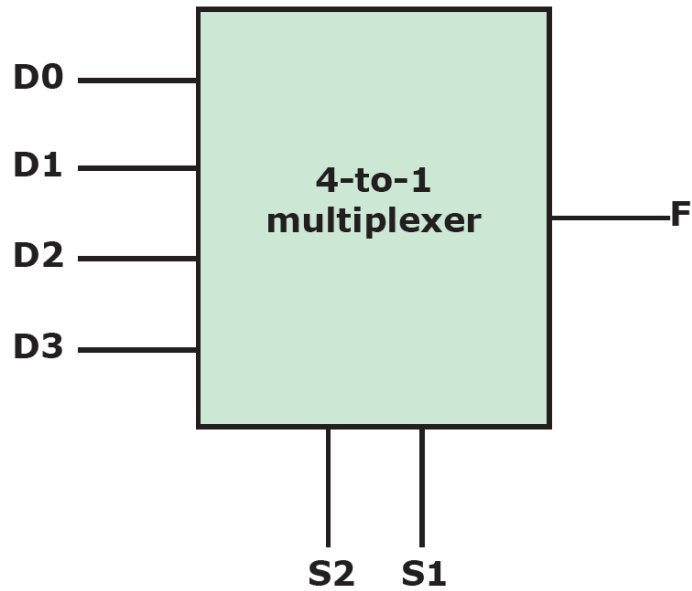

Decoder

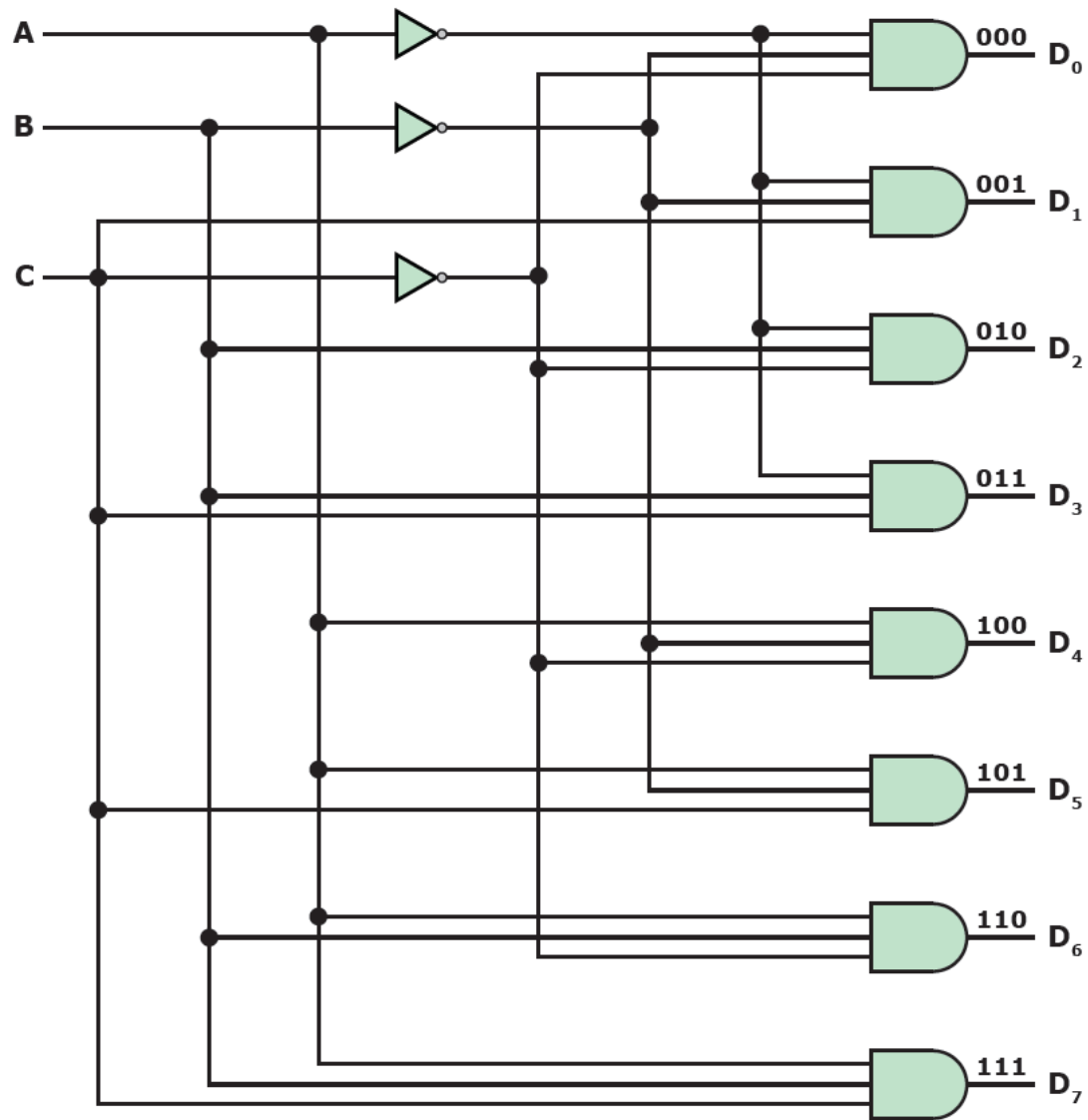


Use of Decoders

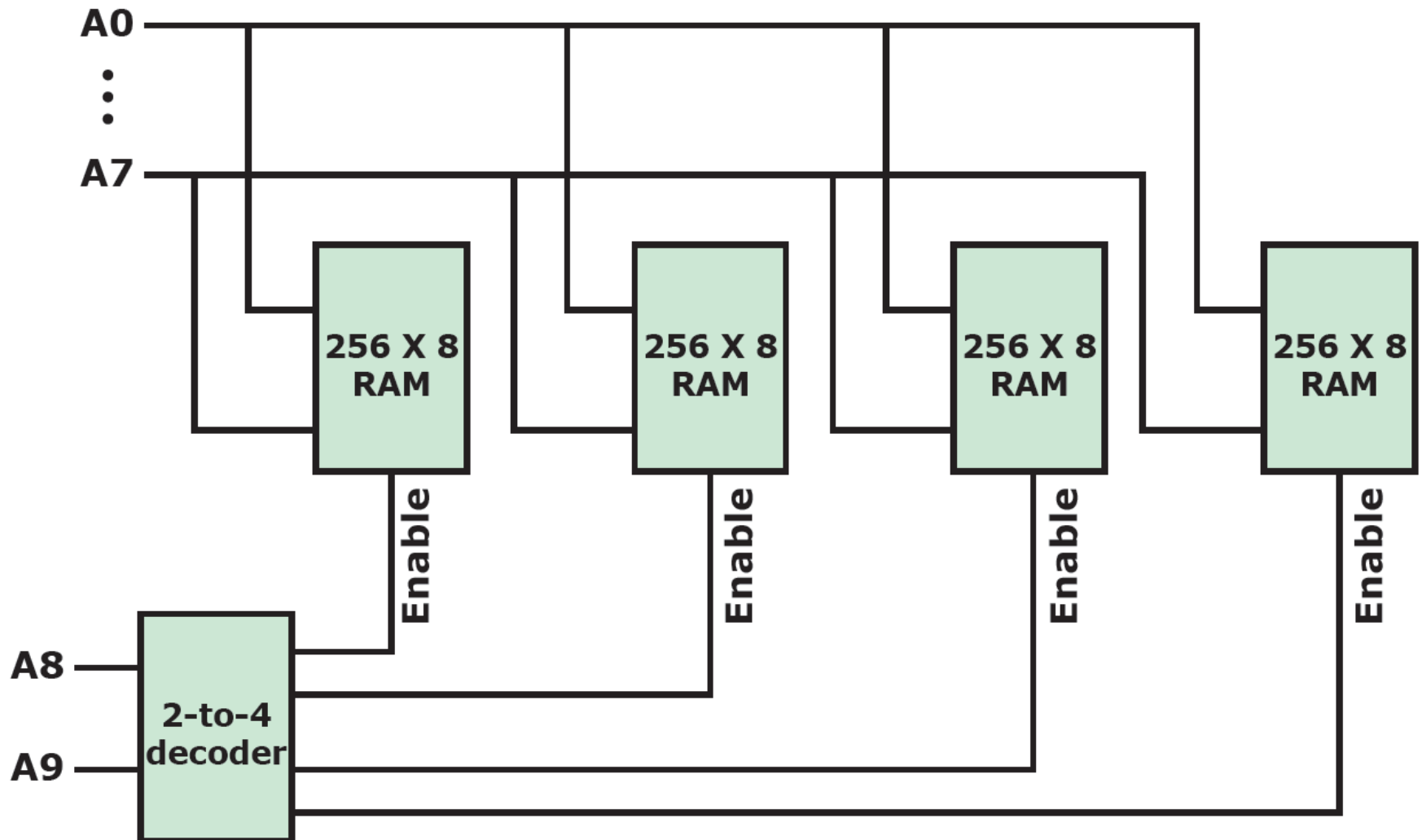

Truth Table of A One Bit Adder

| C_{in} | A | B | Sum | C_{out} |
|----------|---|---|-----|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Combined One Bit Adder

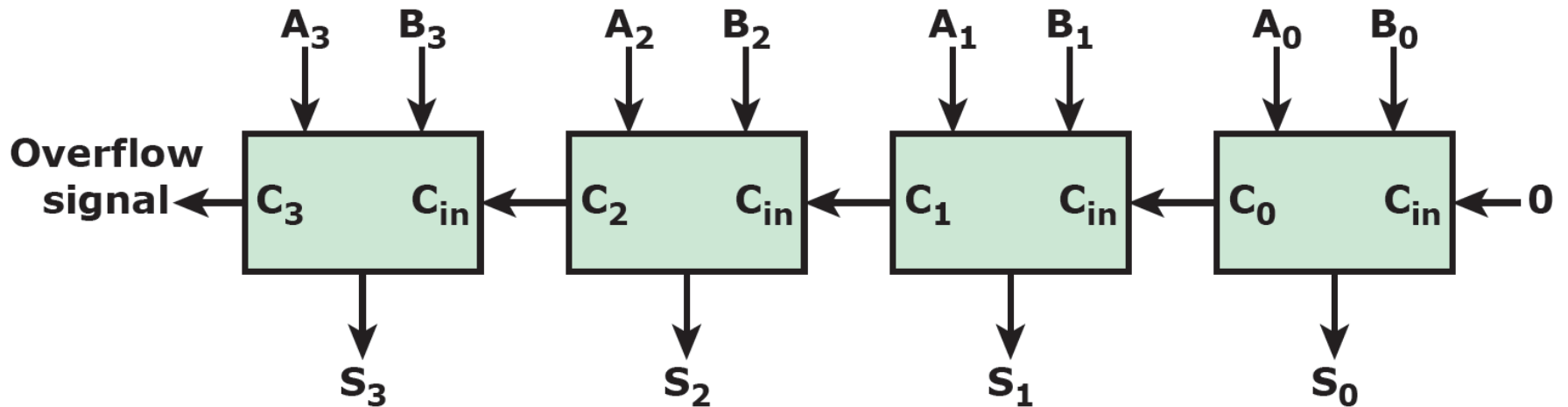

Problems with this Design

- Each Adder has to wait for the Carry signal of the other adders
- This delay becomes unacceptable for larger adders

Problems with this Design

- Each Adder has to wait for the Carry signal of the other adders
- This delay becomes unacceptable for larger adders

Carry Look Ahead:

- For each bit, we can already determine the carry bit:

$$C_0 = A_0B_0$$

$$C_1 = A_1B_1 + A_1A_0B_0 + B_1A_0B_0$$

$$C_2$$

$$= A_2B_2 + A_2A_1B_1 + A_2A_1A_0B_0 + A_2B_1A_0B_0 + B_2A_1B_1 \\ + B_2A_1A_0B_0 + B_2B_1A_0B_0$$

Problems with this Design

Carry Look Ahead:

- For each bit, we can already determine the carry bit:

$$C_0 = A_0B_0$$

$$C_1 = A_1B_1 + A_1A_0B_0 + B_1A_0B_0$$

$$\begin{aligned} C_2 &= A_2B_2 + A_2A_1B_1 + A_2A_1A_0B_0 + A_2B_1A_0B_0 + B_2A_1B_1 \\ &\quad + B_2A_1A_0B_0 + B_2B_1A_0B_0 \end{aligned}$$

- Each carry bit can be expressed this way in a SOP
- They are getting increasingly complex:
 - A n-Bit adder requires $2^n - 1$ AND gates and an OR gate with $2^n - 1$ inputs
 - This is normally only done up to 8 Bit
 - Larger Adder are then built of 8-Bit adders



Digital Logic

Lecture Content

- Boolean Algebra
- Gates & Circuits
- Combinational Circuits
- Minimizing Circuits
- **Sequential Circuits**


Sequential Circuits

- Combinatorial Circuits implement most important function of computers
- But they are state-less, thus they only depend on the input
- No memory function available
- Sequential Circuits:
 - The current output depends on the current input and the current state of that circuit



Flip-Flop

- Simplest form of sequential circuit
- There are a variety of flip-flops, all of which share two properties:
 - The flip-flop is a bistable device. It exists in one of two states and, in the absence of input, remains in that state. Thus, the flip-flop can function as a 1-bit memory.
 - The flip-flop has two outputs, which are always the complements of each other.

S-R Latch

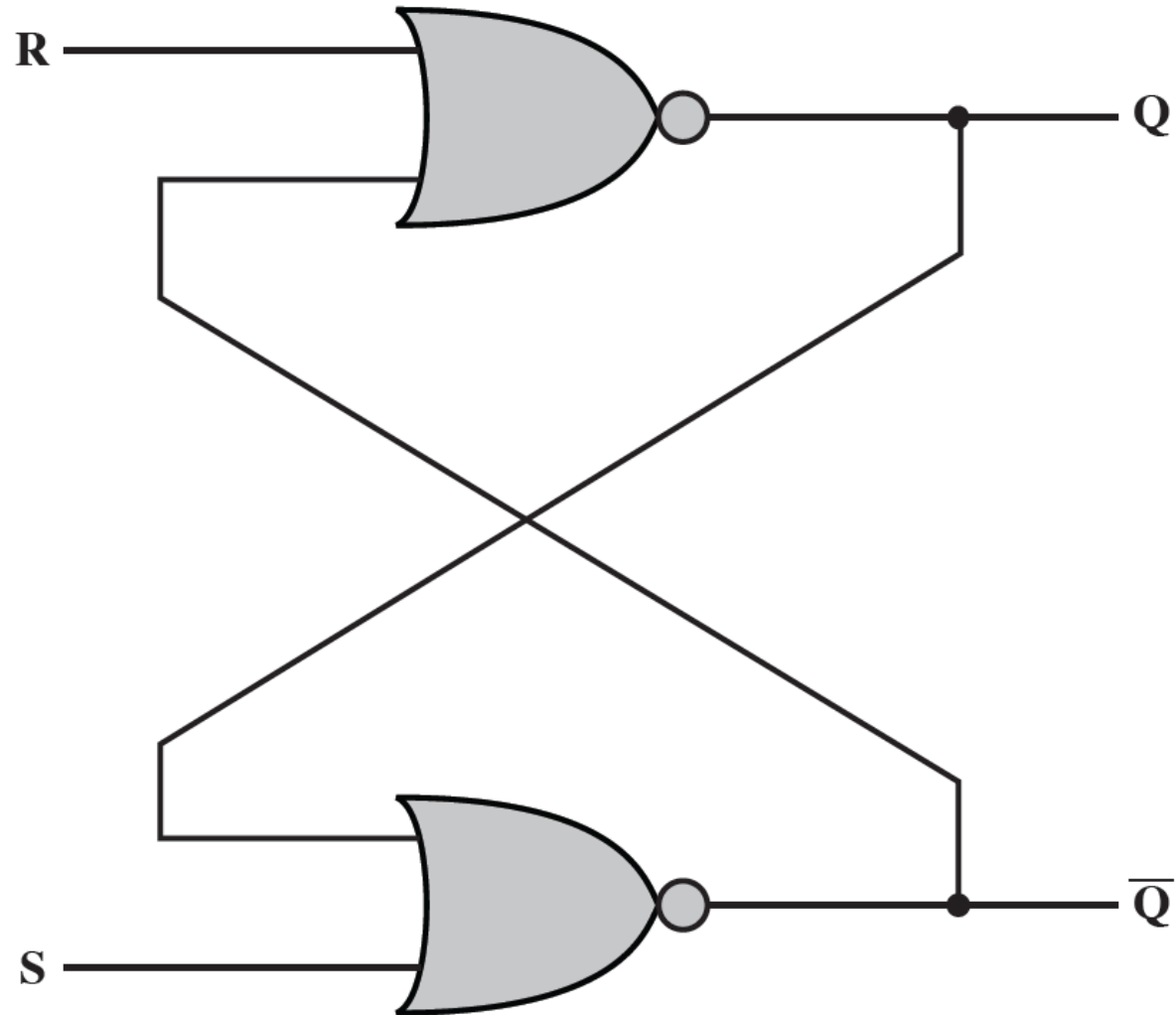

S-R Latch

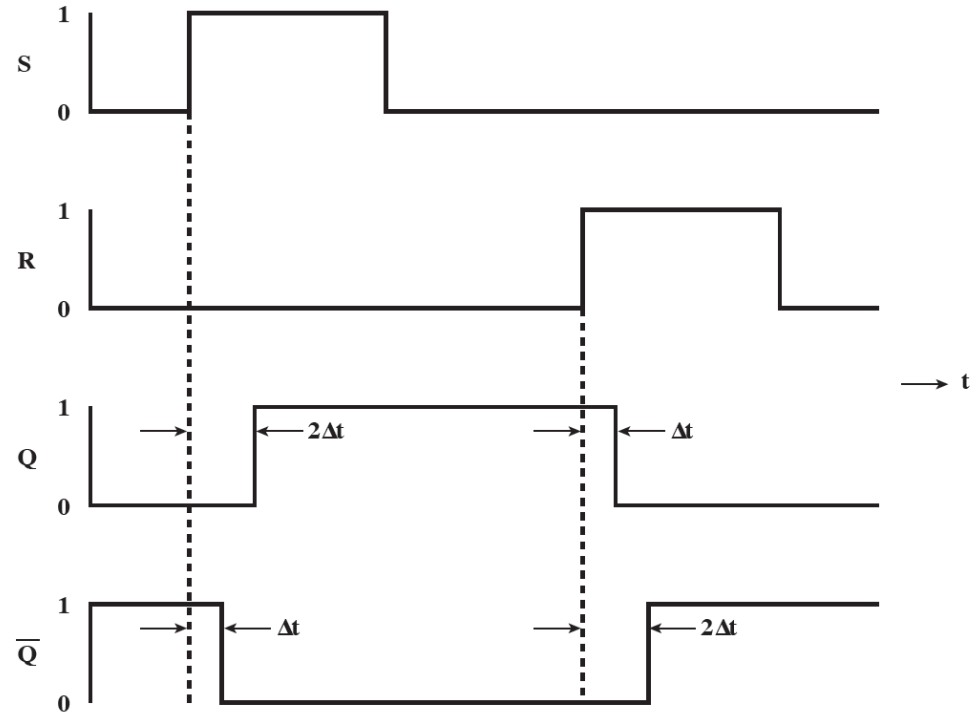
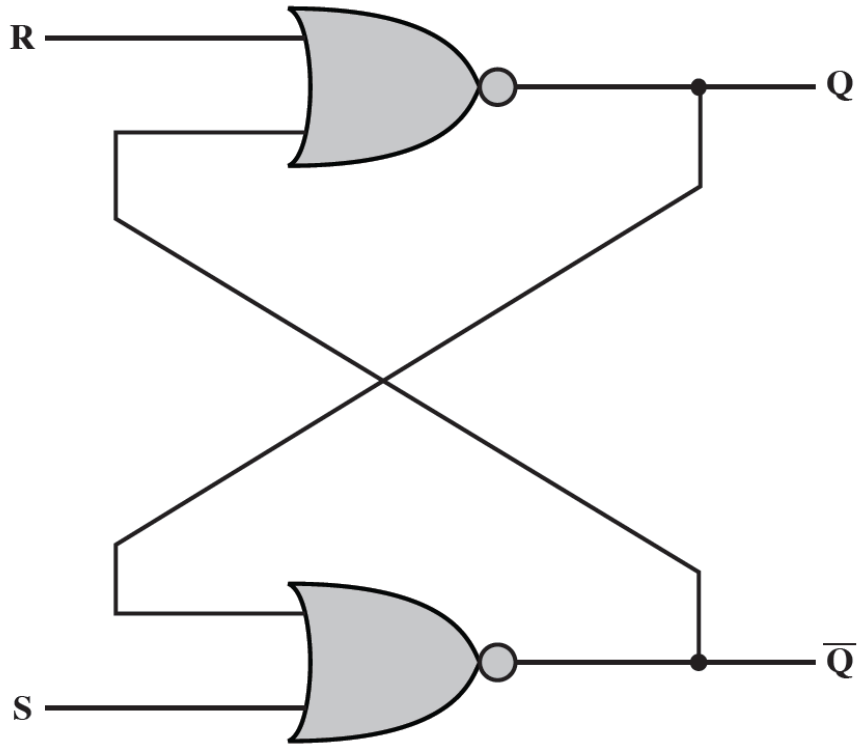


Characteristic Table of the S-R Latch


| SR | Q_n | Q_{n+1} |
|----|-------|-----------|
| 00 | 0 | 0 |
| 00 | 1 | 1 |
| 01 | 0 | 0 |
| 01 | 1 | 0 |
| 10 | 0 | 1 |
| 10 | 1 | 1 |
| 11 | 0 | - |
| 11 | 1 | - |

| S | R | Q_{n+1} |
|---|---|-----------|
| 0 | 0 | Q_n |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | - |




Clocked S-R Flip-Flop & D Flip-Flop

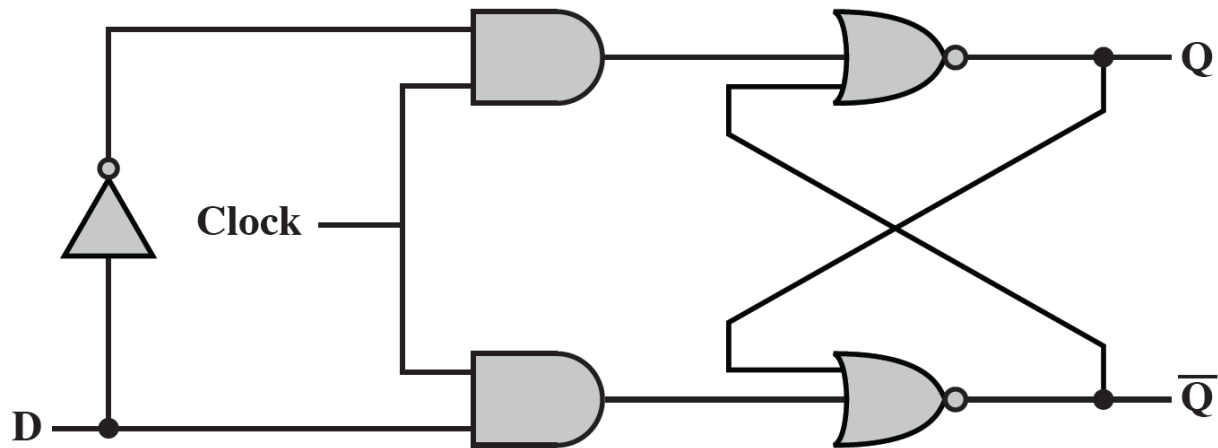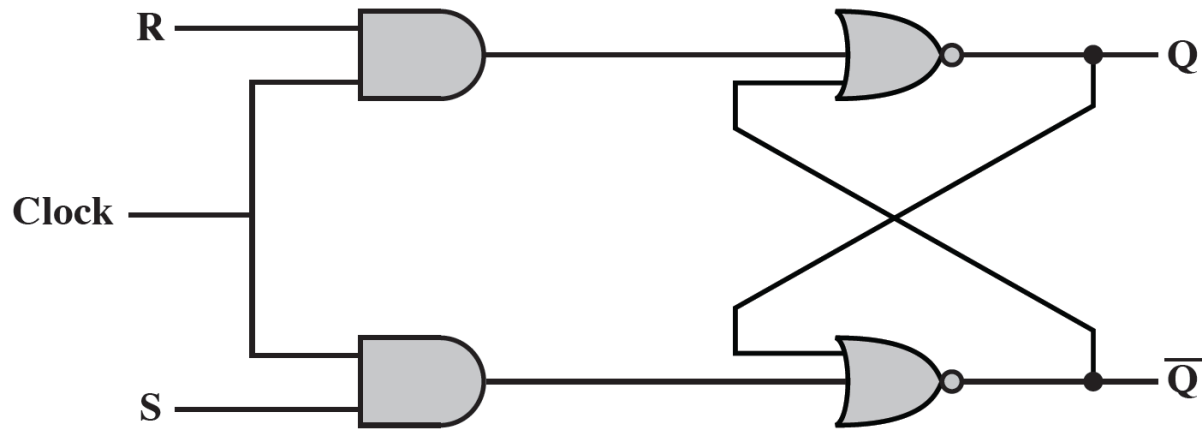


J-K Flip-Flop

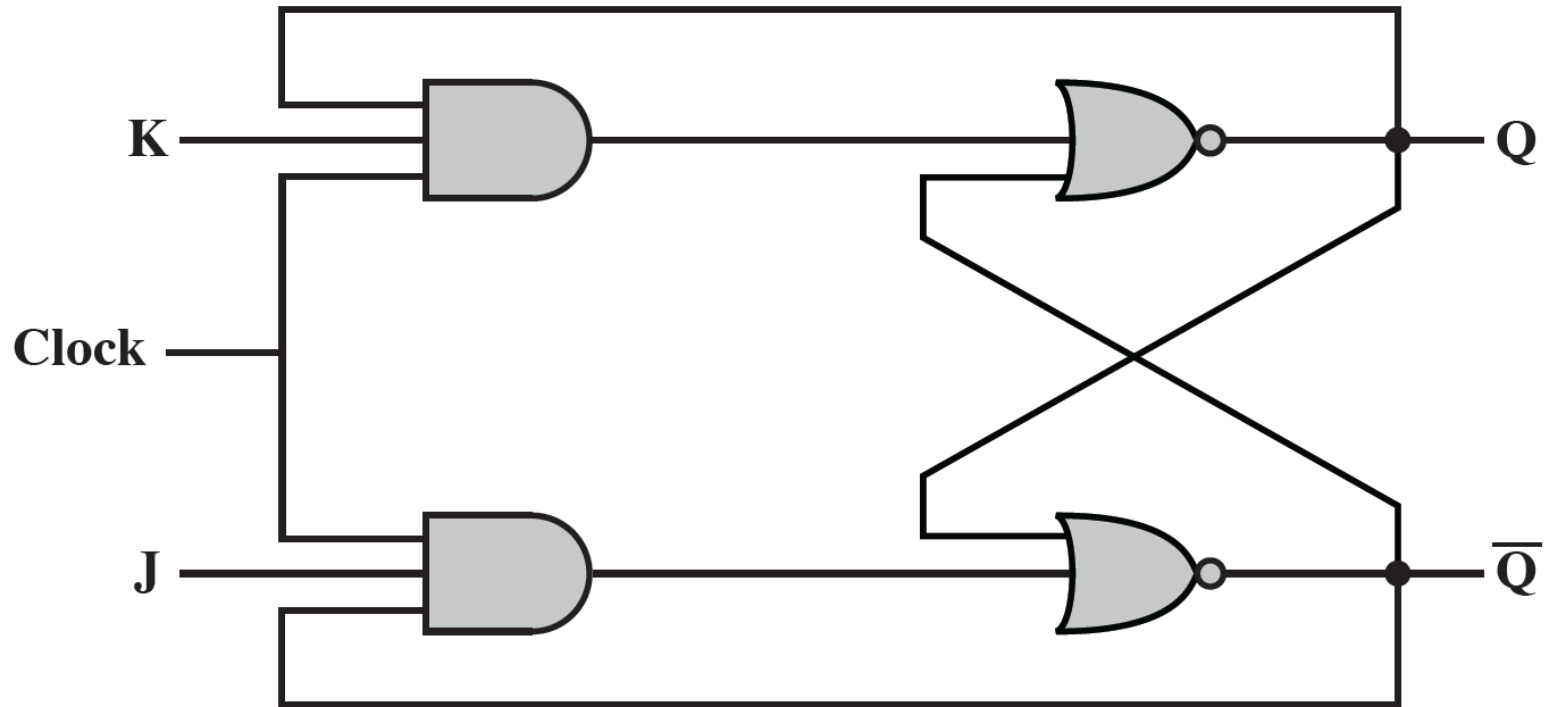

Flip-Flop Overview
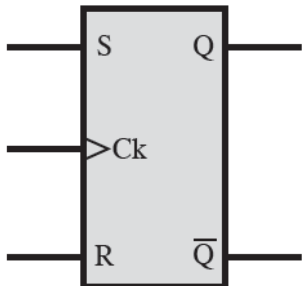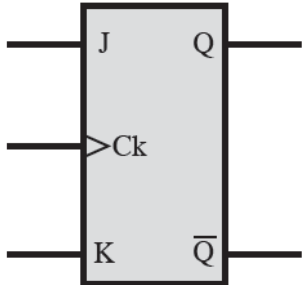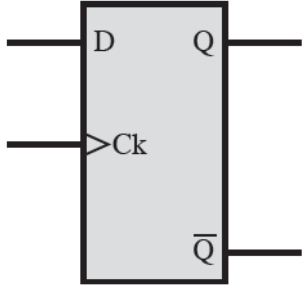
| Name | Graphical Symbol | Truth Table | | | | | | | | | | | | | | | |
|------|---|--|---|-----------|-----------|---|---|-------|---|---|---|---|---|---|---|---|------------------|
| S-R |  | <table><tr><th>S</th><th>R</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>—</td></tr></table> | S | R | Q_{n+1} | 0 | 0 | Q_n | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | — |
| S | R | Q_{n+1} | | | | | | | | | | | | | | | |
| 0 | 0 | Q_n | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | |
| 1 | 1 | — | | | | | | | | | | | | | | | |
| J-K |  | <table><tr><th>J</th><th>K</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>$\overline{Q_n}$</td></tr></table> | J | K | Q_{n+1} | 0 | 0 | Q_n | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | $\overline{Q_n}$ |
| J | K | Q_{n+1} | | | | | | | | | | | | | | | |
| 0 | 0 | Q_n | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | |
| 1 | 1 | $\overline{Q_n}$ | | | | | | | | | | | | | | | |
| D |  | <table><tr><th>D</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table> | D | Q_{n+1} | 0 | 0 | 1 | 1 | | | | | | | | | |
| D | Q_{n+1} | | | | | | | | | | | | | | | | |
| 0 | 0 | | | | | | | | | | | | | | | | |
| 1 | 1 | | | | | | | | | | | | | | | | |

8-Bit Parallel Register

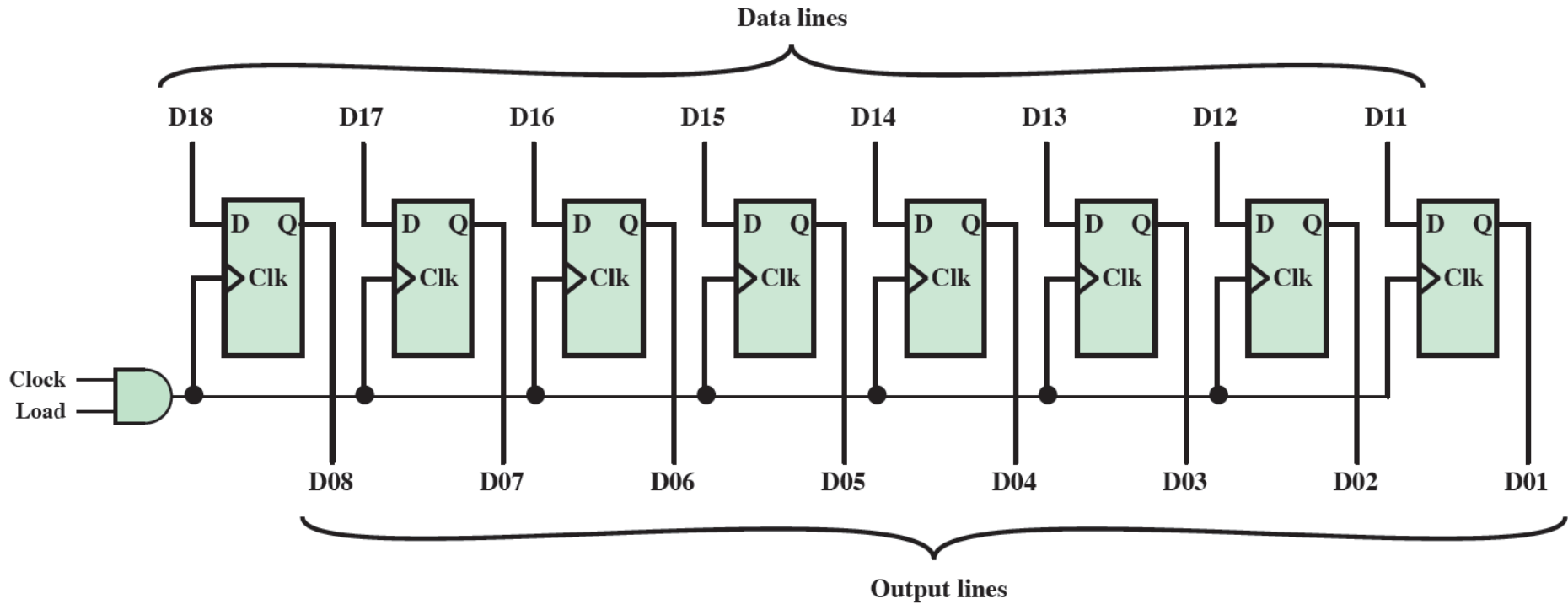

5-Bit Shift Register

